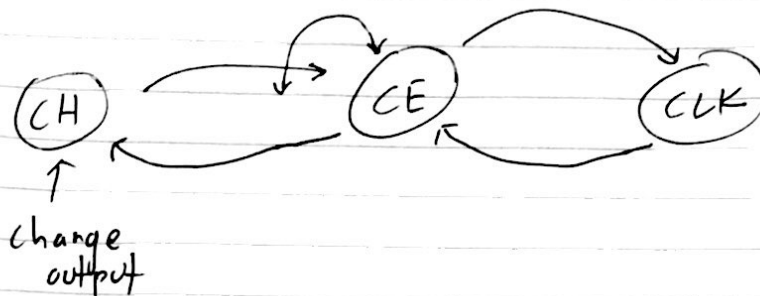


## Lab #10

collab w/ Diana Dang

① Create FSM




Q's

Q1. 8 bits hence minimum states would be 3

Q2. Relationship between state and outputs is dependent on whether or not  $CE=0$ . If  $CE=0$ , output change to 00, 01, 10, 11, 00.

② FSM2.C

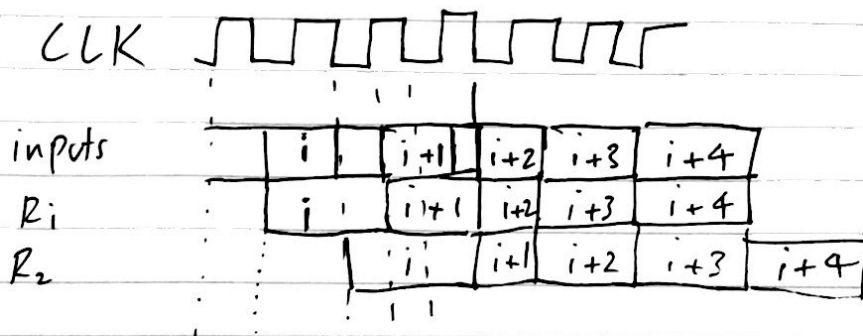

Q3) Register 2  $\rightarrow$  0-8

initial value was 0

Q4) FSM continually adds the 2 values together, 10 times

Q5) FSM 2.C

```

int operation(int a=0; int b=1;) {
    for (int i=0; i<10; i++) {
        a += 1;
        b += 1;
    }
    return a;
}
  
```